


between pins 5 and 6 of the flip-flop has one collector/emitter drop and two diode drops to impress on the leds which, at  $0.1+1.2 = 1.3V$ , is insufficient to turn on one of the leds which stays off if the transistor is good and on if the device has one shorted junction to make it behave like a diode; in this case the voltage drop is  $1.2 + 0.6 = 1.8V$ .

Therefore, one led lights if the transistor is good (both p-n-p and n-p-n); both leds are off for a transistor with shorted C/E junction; and both are on if the transistor is bad. Diodes  $D_{1,2,3,4}$  prevent false indications of normality when a transistor with a B/C short or a B/E short is connected.

**V. Lakshminarayanan**

Centre for Development of Telematics  
Bangalore  
India

state	$D_5$	$D_6$
open C/E	flicker	flicker
short C/E	off	off
good p-n-p	on	off
good n-p-n	off	on

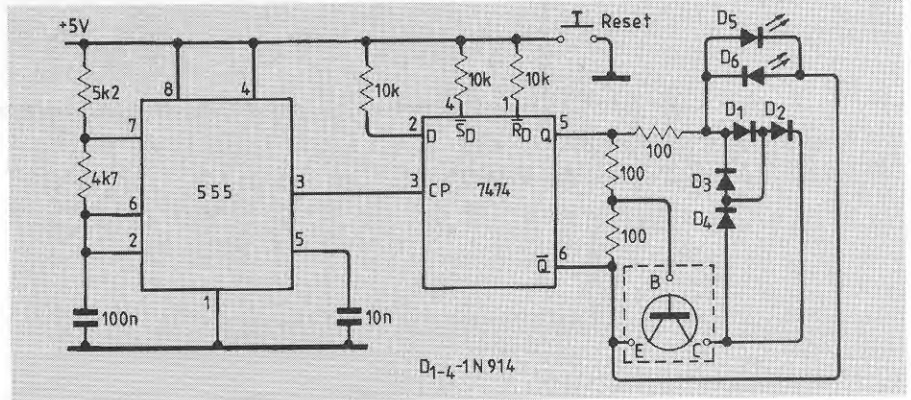

## Single-phase to three-phase converter


This is a method of deriving a three-phase sine-wave reference using a frequency tracking phase-shift network.

In the diagram, the analogue multiplier  $IC_1$ , with R and C, forms a voltage-controlled transfer-function generator, of which the transfer function is

$$(V_o/V_{in})(s) = (V_{CM}RCs)/(10+V_{CM}RCs) \quad (1)$$

where  $V_{CM}$  is the multiplier control voltage.

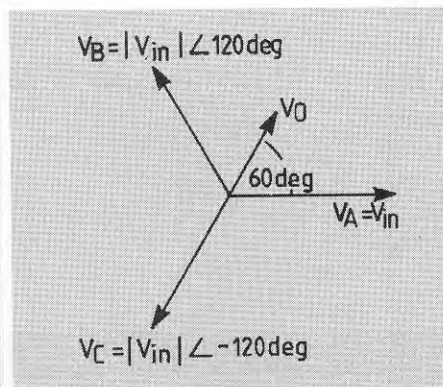The input signal  $V_{IN}$  is half-wave rectified by  $IC_2$  and the multiplier output  $V_O$  is half-wave rectified by  $IC_3$  after being



amplified by a factor of 2 in  $IC_3$ . Integrator  $IC_4$  forms a low-pass filter and high-gain comparator for these two rectified signals, its output being the control voltage  $V_{CN}$  of the multiplier. This feedback loop maintains the magnitude of the transfer function at 0.5 and, under this condition, the phase of the transfer function is exactly  $60^\circ$ .

The phasor diagram shows how the

other two phases are derived from the output of the transfer-function generator. If  $V_A = V_{IN}$  is the reference phase,  $V_O$  has half the amplitude of  $V_A$  and leads it by  $60^\circ$ . In conjunction with the transfer-function generator,  $IC_6$  forms an all-pass network which doubles the phase lead of  $V_O$  while restoring the amplitude to that of  $V_A$  to form the second phase  $V_B$ . The third phase  $V_C$  is formed by inverting  $V_O$  and amplifying it by 2 in instrumentation amplifier  $IC_5$ .

Input to the circuit must be sinusoidal

with no DC offset, although input amplitude is not important. Operation is from 5Hz to 100Hz, distortion is less than 2%, phase error is better than 0.75degrees and the input should be between 1V and 5V.

**Ajoy Raman and K. Radhakrishna Rao**  
Indian Institute of Technology  
Madras

*Editorial survey. Use the information card to evaluate this article. Item K.*

