


## Complementary-pair dc/dc converter simultaneously doubles, inverts supply voltage

Ajoy Raman, Bangalore, India

 The circuit in this Design Idea uses an intrinsic property of collector voltages in one-transformer push-pull dc/dc converters: They have a swing of twice the supply voltage. When you implement these circuits with an NPN device, the collector swings from 0V to twice the supply-rail voltage. When you use PNP devices, the collector voltage swings from  $V_{CC}$  to an equal amplitude but negative  $V_{CC}$  (Reference 1). In this circuit, a complementary pair of transistors, simultaneously imple-

menting a voltage doubler and a negative-voltage source, drives the two windings of the transformer.

One of the windings of transformer  $T_1$  connects to ground, driven by PNP transistor  $Q_1$  from  $V_{CC}$  (Figure 1). The other winding of  $T_1$  connects to  $V_{CC}$ , and NPN transistor  $Q_3$  drives the lower end to ground.  $Q_2$  and  $Q_4$  drive  $Q_1$  and  $Q_3$ , respectively. The collectors of  $Q_3$  and  $Q_1$  through resistors  $R_4$  and  $R_3$  provide cross-coupled drives to  $Q_2$  and  $Q_4$ .  $R_1$  and  $R_2$  form the collector loads for  $Q_2$

### DIs Inside

46 Adjust power-efficient LED switch to any light intensity

47 Obtain a gain of 450 from one vacuum tube

48 Probing system lets you test digital ICs


► To see and comment on all of EDN's Design Ideas, visit [www.edn.com/designideas](http://www.edn.com/designideas).

and  $Q_4$ .  $D_1$  and  $D_4$  prevent the reverse breakdown of  $Q_1$  and  $Q_3$ . The drive configuration and the transformer's winding polarity provide regenerative feedback and self-oscillation so that the transformer alternates between positive and negative saturation, inducing voltages to drive transistors  $Q_1$  and  $Q_3$  alternately on and off.

A square wave with an amplitude twice  $V_{CC}$  is generated at the collector of  $Q_1$ , which swings nominally from  $V_{CC}$  to the equal but negative output voltage. Simultaneously, a square wave with an amplitude twice the supply-rail voltage is generated at the collector of  $Q_3$ , which swings nominally from 0V to twice the supply-rail voltage.

$D_2$  and  $C_2$  provide half-wave rectification and filtering of the  $Q_1$  collector waveform generating the negative voltage output. Half-wave rectification and filtering of the  $Q_3$  collector waveform using  $D_3$  and  $C_3$  generate the doubler's output.

$T_1$  is 200 turns of bifilar AWG 37 enameled wire

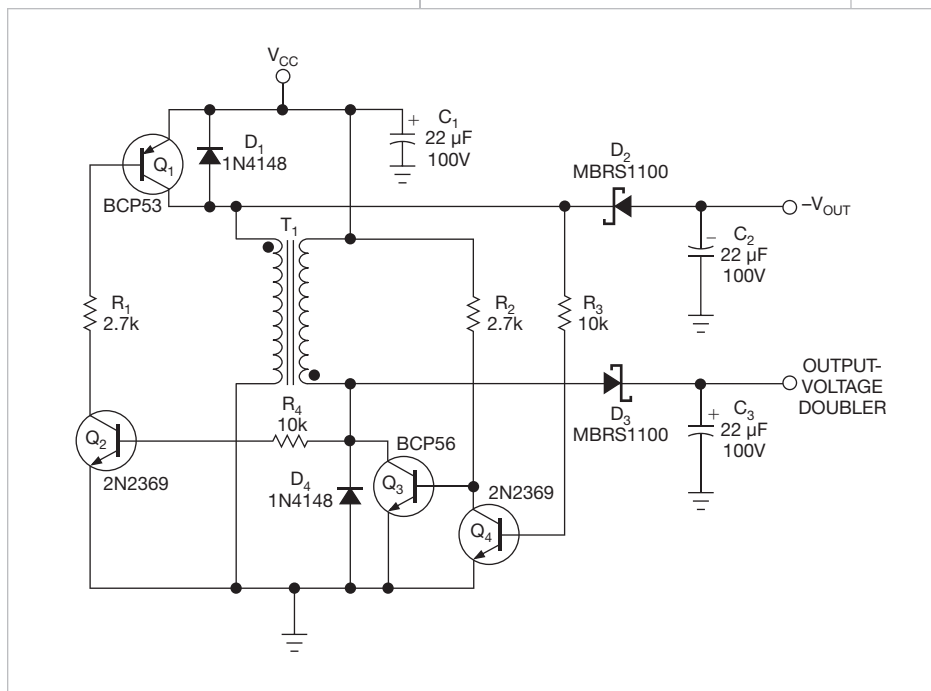

**Figure 1** Cross-coupled regeneration drives switching transistors  $Q_1$  and  $Q_3$  and the windings of the transformer. The resulting voltage swings at their collectors are rectified to twice the positive and the negative power-supply rails.

**TABLE 1** EXPERIMENTAL RESULTS

Input voltage (V)	Input current (mA)	Frequency (kHz)	Voltage doubler (V)	Current doubler (mA)	Negative voltage (V)	Negative current (mA)	Input power (W)	Output power (W)	Efficiency (%)
5	253	2.1	7.68	81.7	-3.41	-72.5	1.27	0.87	69
9.97	360	4.05	17.33	115.5	-8.65	-86.5	3.59	2.75	76.6
15	420	6.02	27.2	136	-13.58	-90.5	6.3	4.93	78.2
19.4	400	7.37	34.9	145.4	-18.33	-61.1	7.76	6.19	79.8
25	340	10.47	48.5	97	-23.8	-79.3	8.5	6.59	77.5
30	410	12.07	56.5	113	-27.6	-92	12.3	8.92	72.5

wound 1-to-1 on a ferrite toroid core (references 2 and 3). Table 1 shows the experimental results with the voltage doubler and negative-voltage-generation circuit operating over an input voltage of 5 to 30V, demonstrating operation over a wide input volt-

age range and providing power at both outputs simultaneously at moderate efficiency. **EDN**

### REFERENCES

1 Raman, Ajoy, "Voltage doubler uses inherent features of push-pull dc/dc


converter," *EDN*, Aug 16, 2007, pg 72, <http://bit.ly/GTlveF>.

2 "T503125," Ceramic Magnetics Inc, <http://bit.ly/L3FzeW>.

3 MN60 manganese-zinc material specs, Ceramic Magnetics Inc, <http://bit.ly/KoyO4Y>.

## Adjust power-efficient LED switch to any light intensity

Raju Baddi, Tata Institute of Fundamental Research, Pune, India


 You can use an LED as a photoelectric sensor. A previous Design Idea shows that such a switch is highly power-efficient, consuming almost no power (Reference 1). However, you cannot adjust that configuration to switch at the desired light intensity while retaining almost the same power efficiency of the original circuit (Figure 1).

Illuminating the reverse-biased green LED with ambient light causes the small current that flows through the LED to form the base current of the BC549 NPN transistor, which is amplified and passed on to the base of the BC177 PNP transistor. A magnified version of this current flows through the emitter of the BC177. The voltage drop across the emitter resistor depends on its value and the current flowing through it, which in turn determines the voltage drop across the CE terminals of the BC549.

By adjusting the value of the series emitter resistor you can set a voltage

corresponding to logic zero of a CMOS gate for any desired intensity of light falling on the green LED. This intensity depends heavily on the response of the green LED and the current gains of the

two transistors, so you select the resistor value by shorting out combinations of the series string of resistors and use the 10-M $\Omega$  potentiometer as a fine adjustment. Once you find a suitable value,

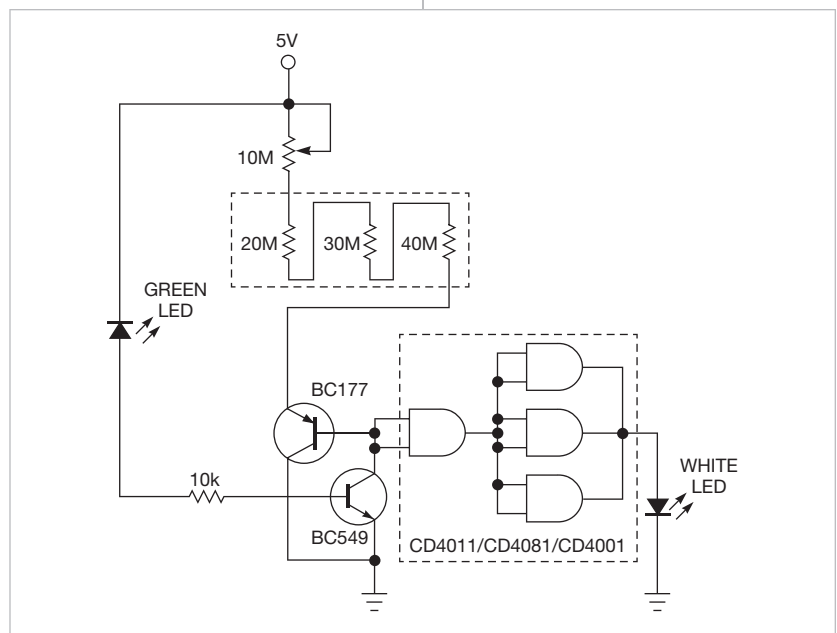

**Figure 1** The photocurrent through the green LED amplifies to CMOS-logic levels to turn on the white LED when ambient light falls.