

Two-quadrant multiplying DAC utilizes octal CMOS buffer

Ajoy Raman - September 30, 2013



Utilizing the large operating voltage range of an octal CMOS buffer, this Design Idea presents a simple 8-bit two-quadrant multiplying Digital-to-Analog-Converter (DAC) built with the buffer/line-driver IC 74HC244.


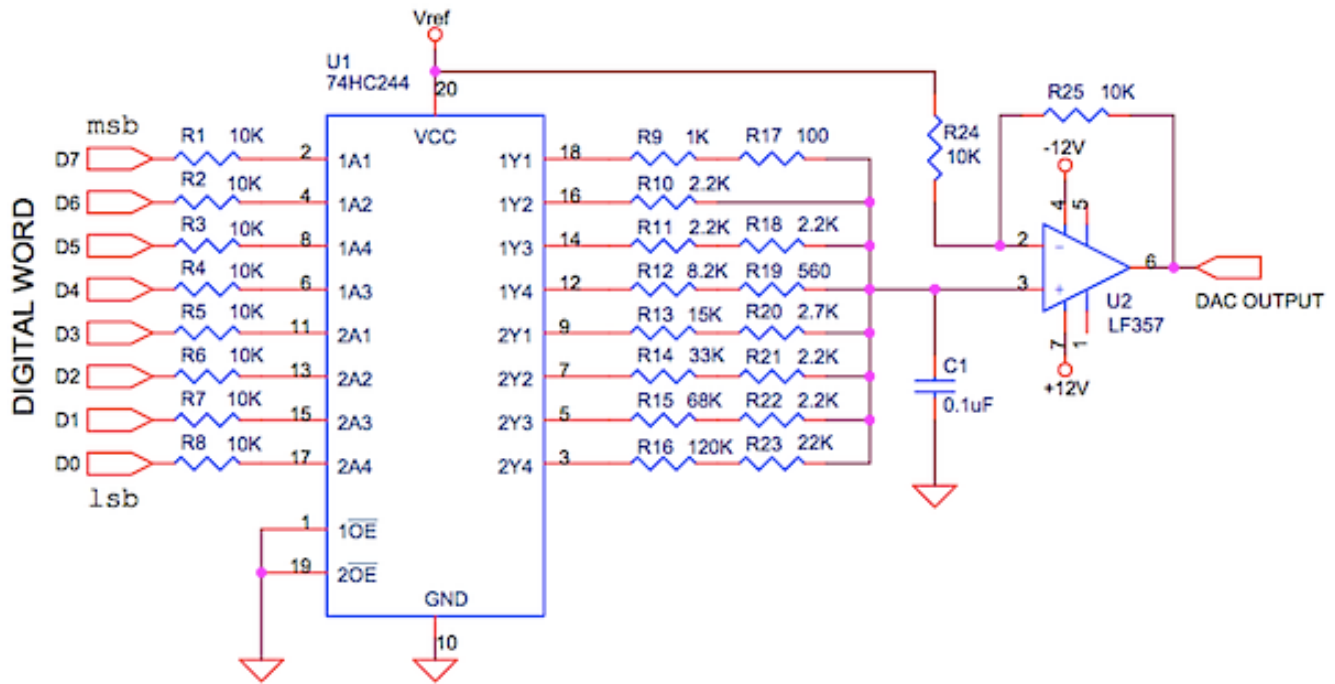


Figure 1

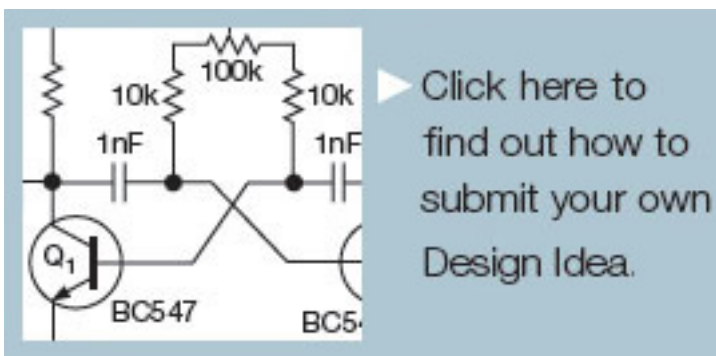

In **Figure 1**, an 8-bit digital word is fed through resistors R1-R8 to the eight inputs of the CMOS buffer U1. The outputs of U1 are combined through a 1:2:4:8...128 weighted resistor network formed by resistors R9-R23. The DAC reference voltage Vref is fed to U1 VCC. The outputs of U1 thus track Vref. Resistors R1-R8 are required to prevent the output voltages of U1 from being influenced by the voltage-levels of the digital inputs.

An 8-bit voltage-output *unipolar* DAC with Vref=VCC is formed at pin 3 of U2. C1 optionally low-pass filters this output, which is buffered, amplified by a factor two, and offset by Vref, to provide a *bipolar* DAC output at pin 6 of the op-amp, an LF357.

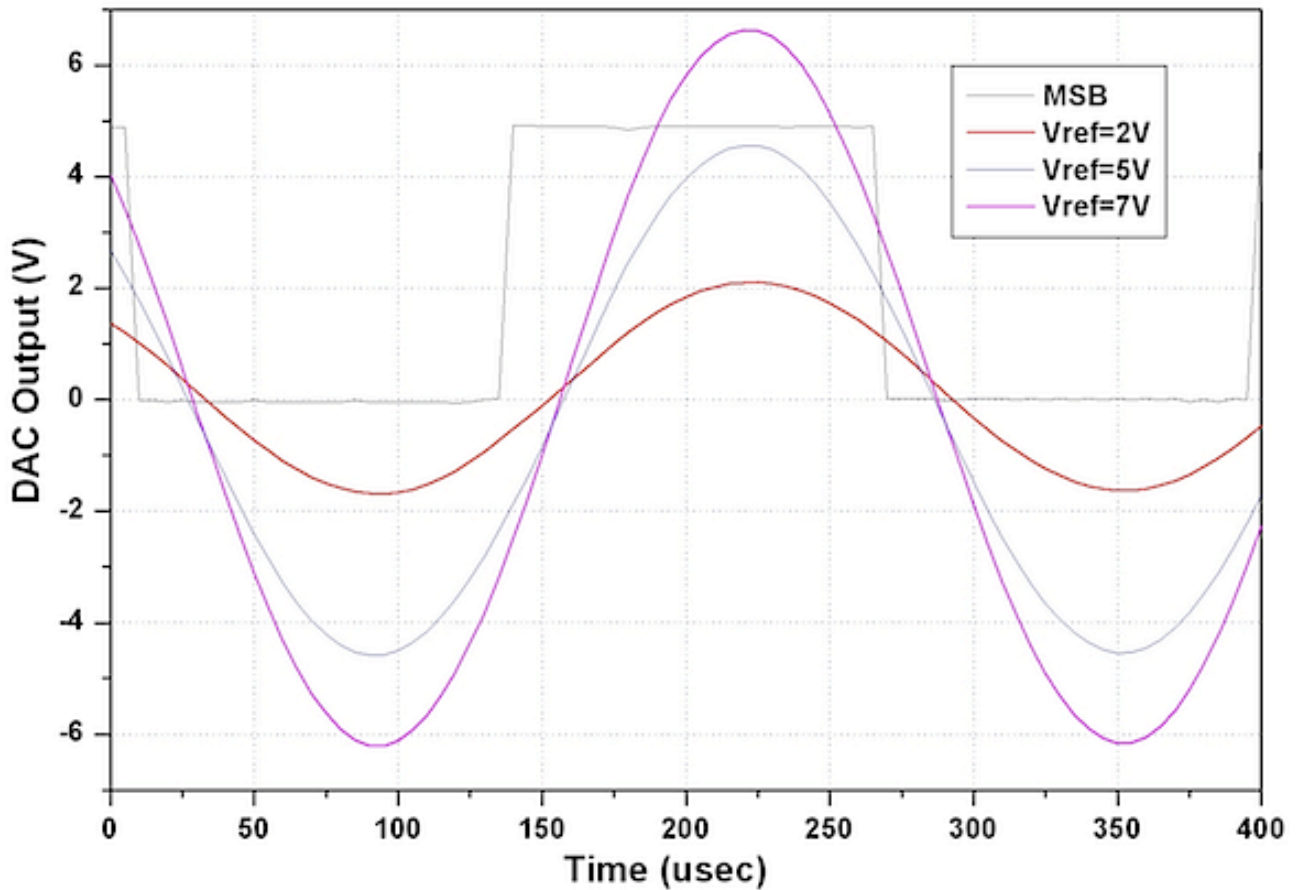


Figure 2 shows the DAC output for a 16-samples/cycle, 3750Hz synthesized sine wave for values of Vref from 2V to 7V. The measured settling time of this DAC is 200ns with $C1 = 200\text{pF}$.

Also see:

- Multidecade BCD DAC uses resistors of only six values
- Flatten DAC frequency response
- Fast-settling synchronous-PWM-DAC filter has almost no ripple